

COMP 303 - TERM PROJECT REPORT

This project is prepared by:
13.01.2017 - 06:00

Due Date:
13.01.2017 - 06:00


PART 1: ALU Design

In this part, ALU was implemented with the opcodes in the table below.

OPCODE	Instruction	Operation
.0000	sub	$C = A - B$
.0001	add	$C = A + B$
.0010	sll (shift left logical)	$C = A \ll B$
.0011	mult	$C = A * B$
.0100	or	$C = A B$
.0101	xor	$C = A \wedge B$
.0110	and	$C = A \& B$
.0111	slt (set less than)	$C = 0 \text{ IF } (A \geq B) ; 1 \text{ IF } (A < B)$
.1000	sra (shift right arithmetic)	$C = A \ggg B$
.1001	srl (shift right logical)	$C = A \gg B$
.1010	Combiner	
.1011	equal?	$C = (? = A B)$
.1100	not Equal?	$C = \sim(? = A B)$

 
a) **Subtractor:**

For sub instruction, firstly 1 bit subtractor was implemented. Then, 32 bit subtractor was implemented using 1 bit subtractor. One bit subtractor is shown below.



 
b) **Adder**

For add instruction first we implemented 1 bit adder. Then we implemented 32 bit adder using this 1 bit adder. One bit adder is shown below.



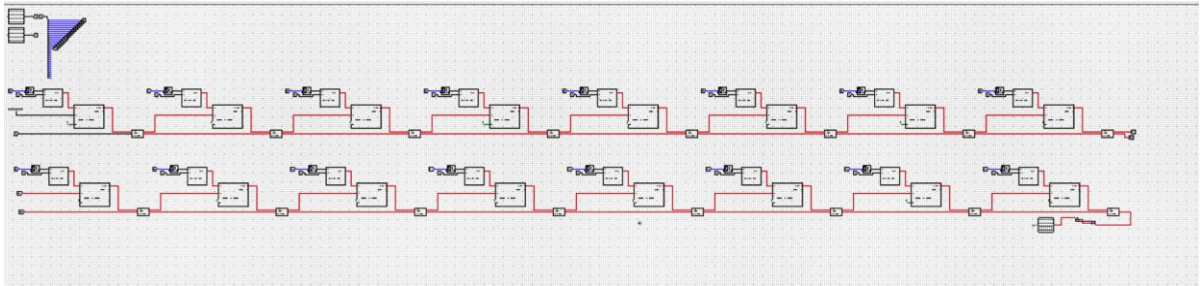c) Multiplier

For MULT op. lecture slides was used which is arithmetic lecture. Multiplier is shown below.



d) XOR, OR, AND

For 'and', 'or' and 'xor', these gates were implemented to all bits of inputs.


e) Shifter

For sl, sea and srl, barrel shifter was used.

 f) Set Less Than (SLT)

For SLT operation first 1 bit SLT implemented than 32 bit SLT implemented. After several logical operations SLT only returns 1 or 0.

Note: When we finish the project, we realize that SLT is broken because of any reason. And there is not enough time to fix it. We hope to get some partial points from this part since we believe that our implementation is mostly correct.



SPECIAL OPERATIONS IN ALU:**g) Combiner**

It combines two inputs and gives it as an output.

 
For example:

Input 1: 0000 0000 0000 0000 0000 0000 0000 0000

Input 2: 1111 1111 1111 1111 1111 1111 1111 1111


Output: 0101 0101 0101 0101 0101 0101 0101 0101

Design of this is shown below.

**h) Equal? and Not Equal?**


Equal? returns 1 if inputs are equal. Its implementation is shown below.

Not Equal? returns 1 if inputs are not equal.

 


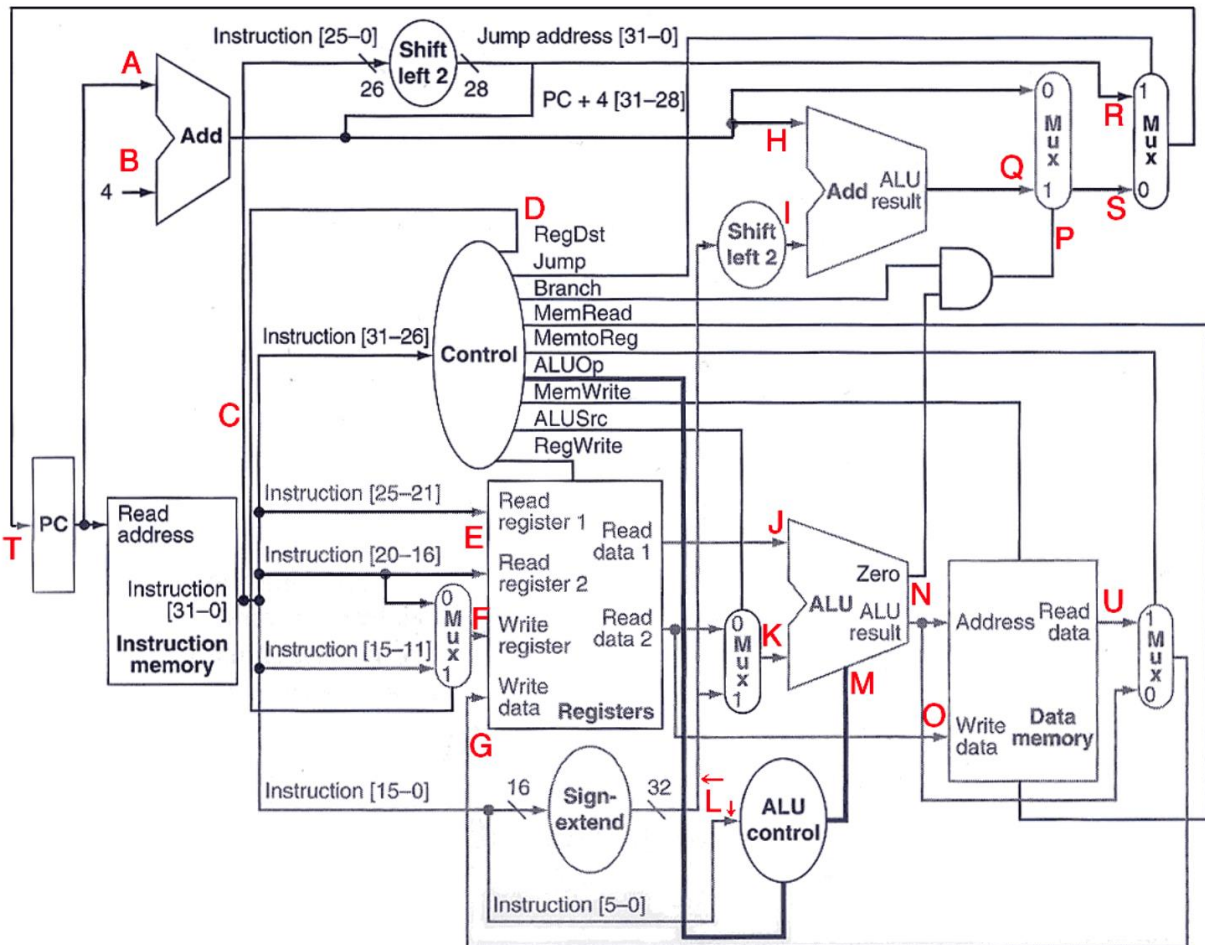PART 2: Single Cycle Processor Design - SCP

In this part, single cycle processor was designed. While processor is being designed, the figure below taken from the lecture book was used as a reference.



Our Design:

 

Our controller and processor was designed according to below operations.


OPCODE	Instruction	Operation
000000	ALU	Arithmetic OP
100011	lw	Load word from memory into register
001011	sw	Store word from register to memory
001100	beq	Branch to a label if two registers are equal
001101	bne	Branch to a label if two registers are not equal
001110	j	Unconditional branch
000000	CUSTOM	CUSTOM METHOD IS IN ALU

As custom instructions, it was designed Combiner, Equal? and Not Equal?. Since they were put in the ALU, they were explained ALU part of this report.


For implementation of the single cycle processor, ALU controller, beq controller and Main Controller were implemented.

a) **ALU Controller:**

ALU Controller is designed as follows.

 


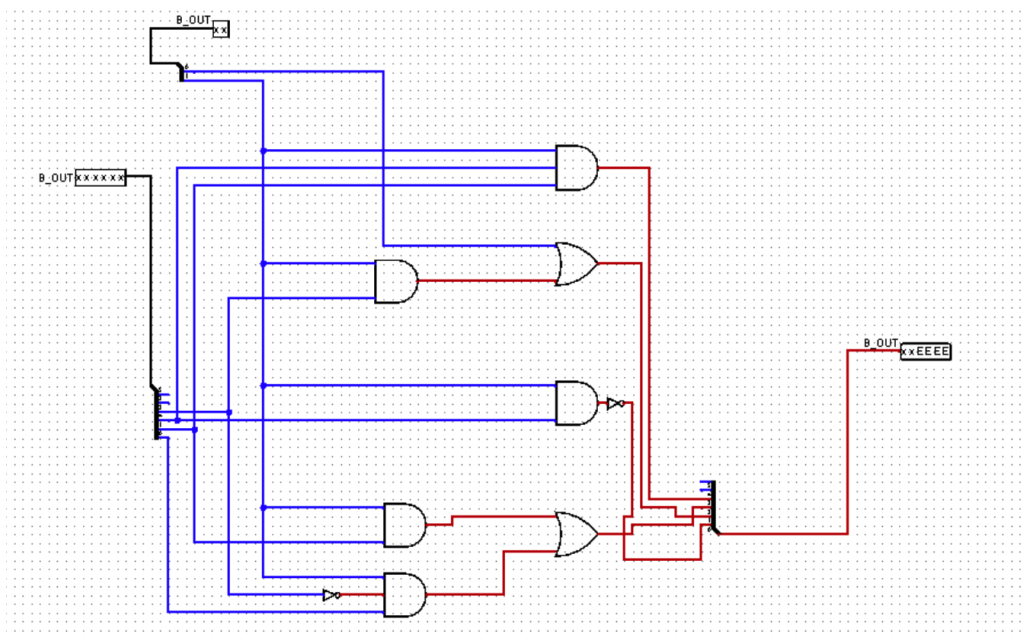At the beginning of the project, ALU controller was designed as below. It was found only this design for ALU controller which gives 4 bit output. (First two bits are not important). It did not work correctly. Thus, the one above was used. This is very simple, but it works correctly for our usage.




b) Main Controller

Main controller was designed as below.

 

c) Beq Controller

This additional controller was design to handle jump, beq and bne. This box returns true only if there will be a jump. Equal and Not Equal boxes were designed in ALU.

 

PART 3: TEST

In this part, two sample code was implemented.

All instructions in this project are working. However, in test part, only lw, sw, J, add, addi, mult, sll, slt and beq were implemented. These are almost all of the instructors. Test codes are as fallows.

a) Test1

In this part, there is a rectangle.

Length of the rectangle was loaded from memory to a \$3.

\$1 is set to 1.

Hight of the rectangle is written to \$2 as 15.

Then, area of the rectangle is calculated by multiplying values in \$2 and \$3.

Area of the rectangle is written to \$4.

Also, sum of the values in \$2 and \$3 is calculated and written to \$5.

Then, value in \$5 is shifted left to obtain circumference of the rectangle.

MIPS LANGUAGE	HEXADECIMAL FORM
J 6	38000006
-- no operation	00000000
-- no operation	00000000
-- no operation	00000000
-- no operation	00000000
-- no operation	00000000
lw \$3, 16(\$2)	8c430004
addi \$1 \$0 1	20010001
addi \$2 \$0 15	2002000F
mult \$4 \$3 \$2	00622030
add \$5 \$2 \$3	00432821
sll \$5 \$5 \$1	00A12810
sw \$3, 0(\$0)	D4030000

b) Test2

Java Version	MIPS LANGUAGE	HEXADECIMAL FORM
<pre>int sum = 0; int number = 0; while (sum<100) { sum=sum + (number * number); number = number + 1; };</pre>	<pre>addi \$1 \$0 1 addi \$2 \$0 100 mult \$4 \$6 \$6 add \$5 \$5 \$4 addi \$6 \$6 1 stl \$s3 \$s2 \$s5 beq \$3 \$1 2</pre>	<pre>20010001 20020064 00C62030 00A42821 20C60001 00451838 30610002</pre>